

EXPERIMENT: -1

AIM OF THE EXPERIMENT:


To study and plot V-I characteristics of SCR.

APPARATUS REQUIRED:

SL No.	Name of Apparatus	Specification	Quantity
1	SCR Trainer		
2	Mains supply		
3	DC power supply		
4	Voltmeter		
5	Ammeter		
6	Patch cords		

THEORY

A thyristor is a four-layer semiconductor device of PNPN structure with three PN junctions. It has three terminal anode, cathode and gate. When the anode voltage is made positive with respect to cathode, the junctions J_1 and J_3 are forward biased. The junctions J_2 is reversed biased and, only a small leakage current flows from anode to cathode. The thyristor is then said to be in the OFF mode. If a Anode to Cathode voltage is increased to a sufficiently large value, the reversed biased junction J_2 will break. This is known as avalanche breakdown and the corresponding voltage is called forward breakdown voltage VBO. Since junctions J_1 and J_3 are already forward biased, there will be free movement of carriers across all three junctions, resulting in a large forward anode current. The device will then be in a conducting state or on state. The voltage drop would be due to the ohmic drop in the four layers and it is small, typically, 1V. In the on state, the anode current is limited by an external impedance or resistance.

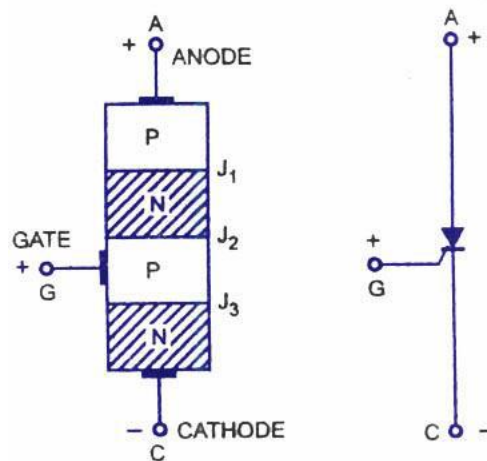

CONCLUSION

Sign. of the Student

Sign. of the faculty

EXPERIMENT: - 2

AIM OF THE EXPERIMENT

To study the cosine-controlled triggering circuit

APPARATUS REQUIRED

SL No.	Name of Apparatus	Specification	Quantity
1	Cosine Trainer Kit		
2	Mains supply		
3	DC power supply		
4	Multimeter		
5	Ammeter		
6	DSO		
7	Patch cords		

THEORY

The synchronizing transformer steps down the supply voltage to an appropriate level. The input to this transformer is taken from the same source from which converter circuit is energized. The output voltage V_1 of synchronizing transformer is integrated to get cosine-wave V_2 . The dc. control voltage E_c varies from maximum positive E_{cm} to maximum negative E_{cm} so that firing angle can be varied from zero to 180° . The cosine wave V_2 is compared in comparators 1 and 2 with E_c and $-E_c$. When E_c is high as compared to V_2 , output voltage V_3 is available from comparator-1. Same is true for comparator-2. So, the comparators 1 and 2 give output pulses V_3 and V_4 respectively as shown in the Fig. It is seen from this figure that firing angle is governed by the intersection of V_2 and E_c . When E_c is maximum, firing angle is zero. Thus, firing angle α in terms of V_{2m} and E_c can be expressed as

$$V_{2cm} \cos \alpha = E_c$$
$$\alpha = \cos^{-1} \left(\frac{E_c}{V_{2cm}} \right)$$

The signals V_3 , V_4 obtained from comparators are fed to clock-pulse generators 1, 2 to get clock pulses V_s , V_G as shown in Fig. These signals V_s , V_G energize a JK flip flop to generate output signals V_i and V_j . The signal V_j is amplified through the circuit and is then employed to turn on the SCRs in the positive half cycle. Signal V_j , after amplification, is used to trigger SCRs in the negative half cycle.


For a single-phase full converter, average output voltage is given by

$$V_0 = \frac{2V_m}{\pi} \cos \alpha$$
$$V_0 = \frac{2V_m}{\pi} \cos \left(\cos^{-1} \left(\frac{E_c}{V_{2cm}} \right) \right)$$


$$V_o = kE_c$$

This shows that cosine firing scheme provides a linear transfer characteristic between the average output voltage V_o and the control voltage E_c . This scheme, on account of its linear transfer characteristic, improves the closed-loop response of the converter system.

MODEL GRAPH

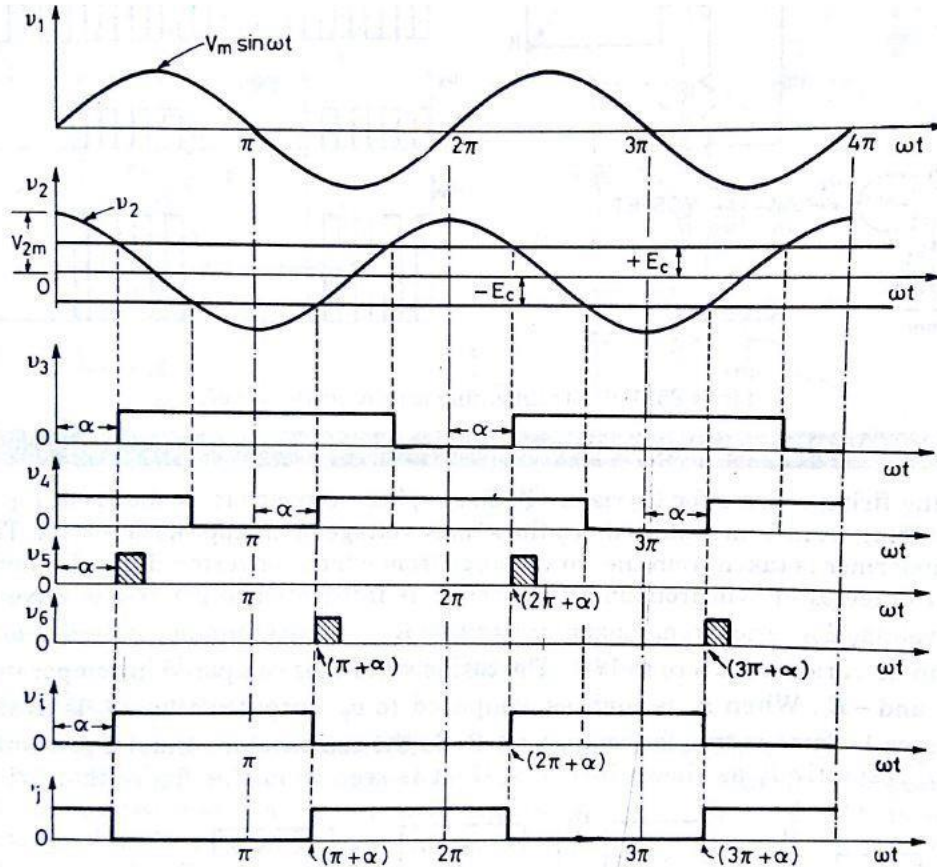

CIRCUIT DIAGRAM

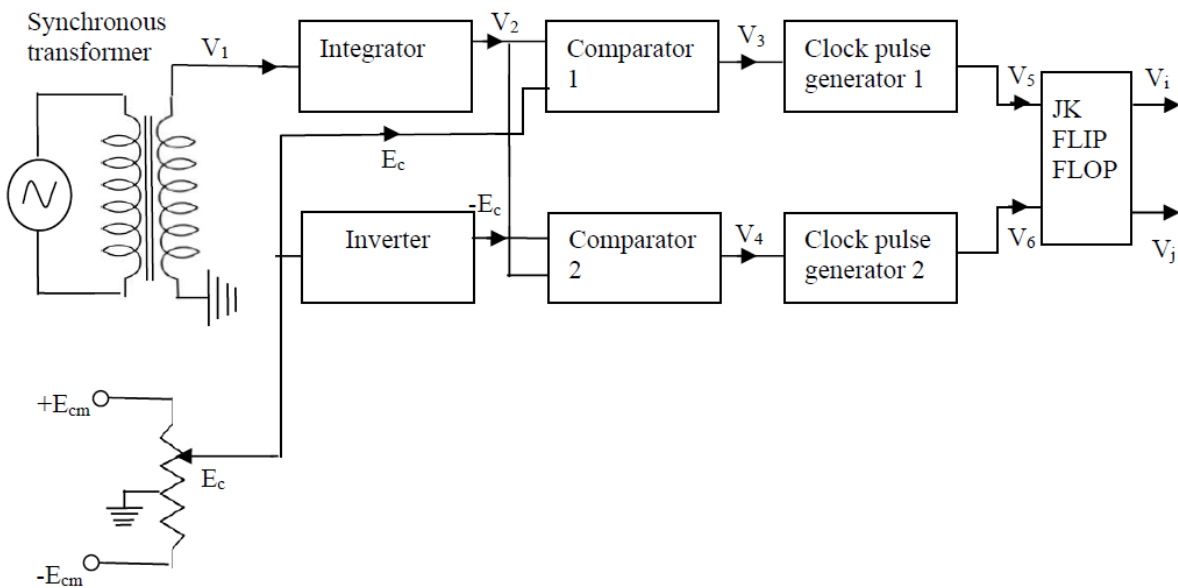

PROCEDURE

1. The power supply was switched on.
2. The DSO was switched on.
3. The pulse realise switch S_1 was switched on.

4. The peak value of AC input voltage E_m and trigger angle α was noted down.
5. The Output voltage V_0 and corresponding firing angle α was observed by varying the pot P_1 .

OBSERVATION TABLE

Sl. No.	Trigger Angle (α)	Output voltage

CONCLUSION

Sign. of the Student

Sign. of the faculty

EXPERIMENT: -3

AIM OF THE EXPERIMENT


To measure the latching and holding current of SCR.


APPARATUS REQUIRED

SL No.	Name of Apparatus	Specification	Quantity
1	SCR Trainer		
2	Mains supply		
3	DC power supply		
4	Voltmeter		
5	Ammeter		
6	Patch cords		

THEORY

A thyristor is a four-layer semiconductor device of PNPN structure with three PN junctions. It has three terminal anode, cathode and gate. When the anode voltage is made positive with respect to cathode, the junctions J_1 and J_3 are forward biased. The junctions J_2 is reversed biased and, only a small leakage current flows from anode to cathode. The thyristor is then said to be in the OFF mode. If a Anode to Cathode voltage is increased to a sufficiently large value, the reversed biased junction J_2 will break. This is known as avalanche breakdown and the corresponding voltage is called forward breakdown voltage V_{B0} . Since junctions J_1 and J_3 are already forward biased, there will be free movement of carriers across all three junctions, resulting in a large forward anode current. The device will then be in a conducting state or on state. The voltage drop would be due to the ohmic drop in the four layers and it is small, typically, 1V. In the on state, the anode current is limited by an external impedance or resistance.

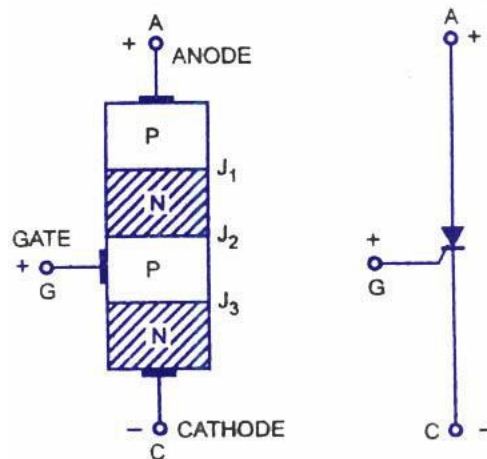

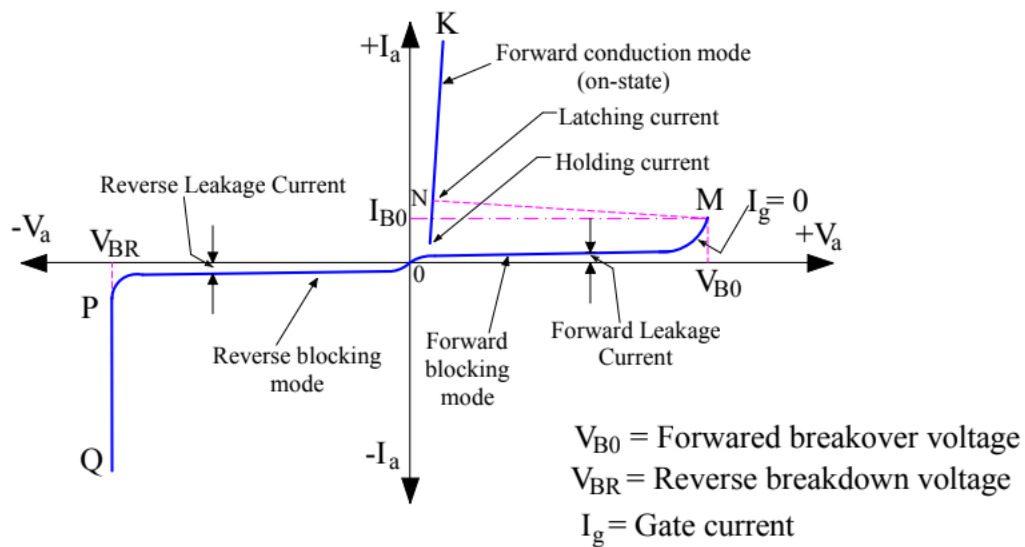

CIRCUIT DIAGRAM

PROCEDURE

To find latching current:

1. R1 was kept at middle position.
2. By varying V_2 20V was applied to the Anode to cathode.
3. The V_g voltage was increased by varying V_a till the device turns ON indicated by sudden rise in I_A .
4. Now R_A was set at maximum position, then SCR turns OFF.
5. Now the R_A was decreased slowly, to increase the Anode current gradually in steps.
6. At each and every step, the gate was made OFF and ON, voltage switches V_a . If the Anode current is greater than the latching current of the device, the device stays ON even after switch S_1 OFF, otherwise device goes to blocking mode as soon as the gate switch is put OFF.
7. If $I_A > I_L$ then, the device remains in ON state that anode current as latching current was recorded.

To find holding current:

1. The load current was increased from latching current level by varying R_A & V_A .
2. The gate voltage switch S_1 was made off permanently (now the device is in ON state).
3. The load resistance (R_2) was increased, so that anode current started reducing, at some anode current the device goes to turn off which was noted down. Take small steps to get accurate holding current value.

OBSERVATION

Latching current = _____ Holding current = _

CONCLUSION

Sign. of the Student

Sign. of the faculty

EXPERIMENT: - 4(a)

AIM OF THE EXPERIMENT

To study the single-phase half wave-controlled rectifier with R and R-L load.


APPARATUS REQUIRED

SLNo.	Name of Apparatus	Specification	Quantity
1	1-phase controlled rectifier trainer kit		
2	Gate triggering circuit		
3	DSO		
4	1-ph Variac		
5	Multi-meter		
6	R and R-L load		
7	Connecting wires		

THEORY

We know that thyristor is a unidirectional device, allowing the flow of current only in one direction. When the thyristor is forward-biased i.e., anode terminal is positive with respect to the cathode terminal, and the gate terminal is not triggered, there will be no conduction due to the reverse biasing of the inner junction of SCR. Hence, the entire supply voltage appears across the SCR. The magnitude of the conduction current depends upon the instant when it is triggered i.e., firing angle ' α ', and the load resistance R. Since the circuit does not contain any energy storing elements, the load current will be in phase with voltage and becomes zero instantaneously with the voltage at zero crossing (at $\omega t = \pi$ rad/sec). The load current and voltage are zero from 0 to α . When SCR is triggered by giving gate signal at α . The entire supply voltage except for drop across SCR will be applied across the load (from $\omega t = \alpha$ to $\omega t = \pi$). At $\omega t = \pi$, the phase reversal takes place and the negative half-cycle of the input supply will start. Due to the negative half-cycle, the SCR will be reverse biased and will be turned OFF at $\omega t = \pi$. From $\omega t = \pi$ to $\omega t = 2\pi$, the load current and voltage will be zero. Again, when the positive half cycle starts i.e., from $\omega t = 2\pi$, SCR will be forward biased but it will not be switched ON until it is triggered i.e., until $\omega t = (2\pi + \alpha)$

MODEL GRAPH

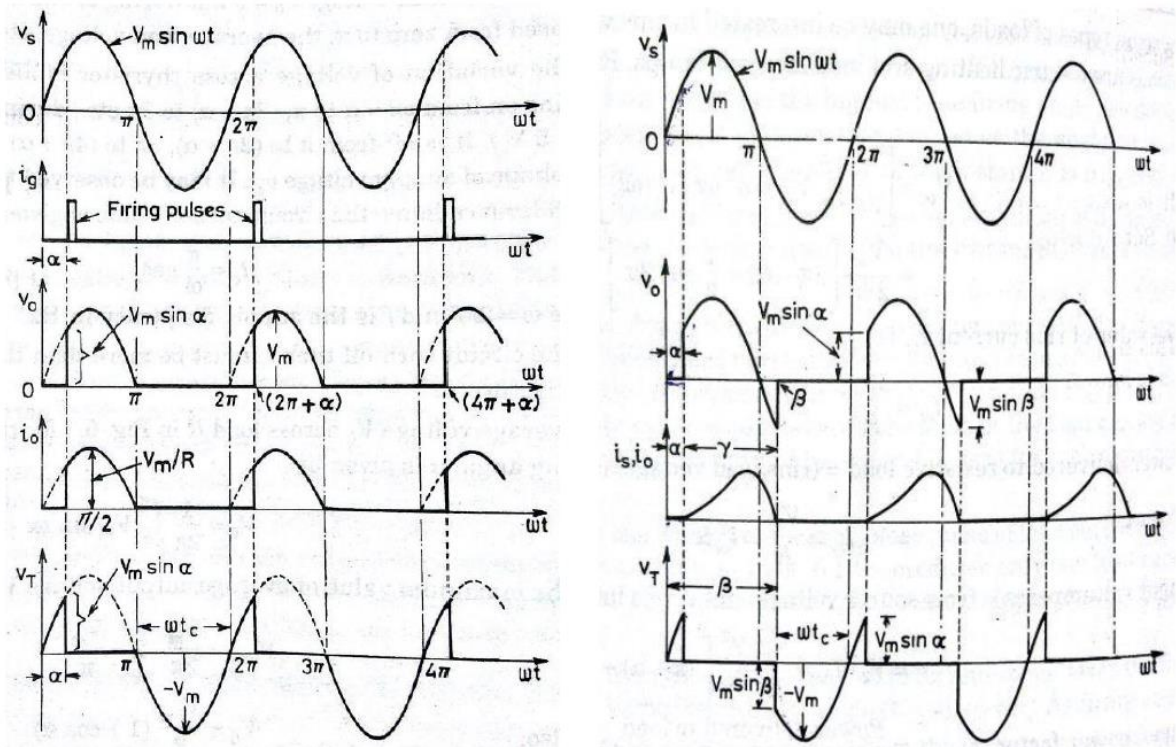

CIRCUIT DIAGRAM

PROCEDURE

1. The Connections were made as per the circuit diagram.
2. The CRO and voltmeter was connected across the load.
3. The potentiometer was kept at the minimum position.
4. AC source was switched on.
5. The output wave form was observed and the output voltage was calculated.

OBSERVATION TABLE

Sl. No.	Firing angle (α)	I/P Voltage (Volts)	O/P Voltage (Volts)

TRACINGS

CONCLUSION

Sign. of the Student

Sign. of the faculty

EXPERIMENT: - 4(b)

AIM OF THE EXPERIMENT

To study the single-phase half wave semi-controlled rectifier with R and R-L load.


APPARATUS REQUIRED

Sl. No.	Name of Apparatus	Specification	Quantity
1	I-phase SCR controlled trainer kit		
2	Gate triggering circuit		
3	DSO		
4	1-ph Variac		
5	Multi-meter		
6	R, R-L, Lamp Load		
7	Connecting wires		

THEORY

The bridge circuit of the semi converter has two diodes (D_1, D_2) and two SCRs (T_1, T_2). Pair of a diode and SCR (D_2, T_1) is connected in the parallel with another pair of a diode and SCR (D_1, T_2). And finally, the bridge circuit has a parallel connection with the RL circuit. Thus, this bridge circuit is the main circuit of the semi converter.

MODEL GRAPH

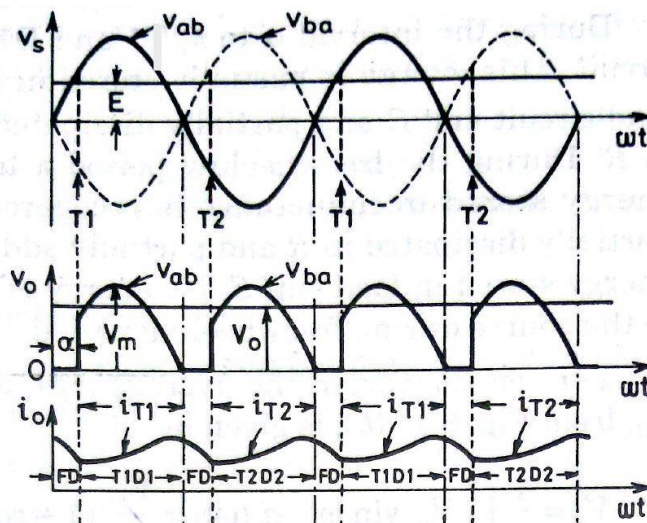

CIRCUIT DIAGRAM

PROCEDURE

1. The Connections were made as per the circuit diagram.
2. The voltmeter and DSO was connected across the load.
3. The potentiometer was kept at the minimum position.
4. AC source was switched on.
5. The output wave form was observed and the output voltage was calculated.

OBSERVATION TABLE

Sl. No.	Firing angle (α)	I/P Voltage (Volts)	O/P Voltage (Volts)

TRACINGS**CONCLUSION****Sign. of the Student****Sign. of the faculty**

EXPERIMENT: -5

AIM OF THE EXPERIMENT

To study single-phase full wave-controlled rectifier circuits (Bridge type) with R-load.

APPARATUS REQUIRED

SL.No.	Name of Apparatus	Specification	Quantity
1	SCR trainer kit		
2	Gate triggering circuit		
3	DSO		
4	1-ph Variac		
5	Multi-meter		
6	Ammeter		
7	Connecting wires		


THEORY

A fully controlled converter uses thyristors only and there is a wider control over the de output voltage. With pure resistive load, it is single quadrant converter. Here, both the output voltage and output current are positive. With the RL-load it becomes a two-quadrant converter. Here, output voltage is either positive or negative but output current is always positive. This type of full wave rectifier circuit consists of four SCRs.

During the positive half cycle, SCRs T_1 and T_2 are forward biased. At $\omega t = \alpha$, SCRs T_1 and T_2 are triggered, then the current flows through the AC+ - T_1 -R load - T_2 -AC-. At $\omega t = \pi$, supply voltage falls to zero and the current also goes to zero. Hence SCRs T_1 and T_2 turned off. During negative half cycle (π to 2π). SCRs T_3 and T_4 are forward biased. At $\omega t = \pi + \alpha$, SCRs T_3 and T_4 are triggered, then current flows through the path AC+ - T_3 -R load - T_4 -AC-. At $\omega t = 2\pi$, the supply voltage and current go to zero, SCRs T_3 and T_4 are turned off. The output voltage is given by

$$V_0 = \frac{V_m}{\pi} (1 + \cos\alpha)$$

MODEL GRAPH

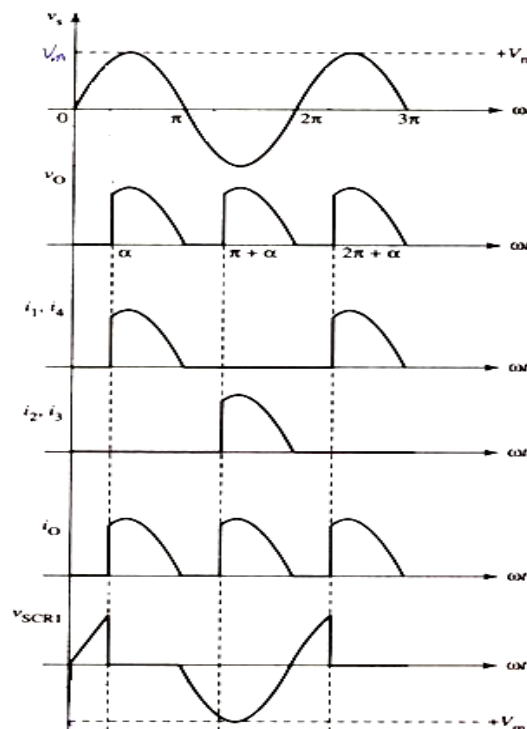

CIRCUIT DIAGRAM

PROCEDURE

1. The Connections were made as per the circuit diagram.
2. The voltmeter and DSO was connected across the load.
3. The potentiometer was kept at the minimum position.
4. AC source was switched on.
5. The output wave form was observed and the output voltage was calculated.

OBSERVATION TABLE

Sl. No.	Firing angle (α)	I/P Voltage (Volts)	O/P Voltage (Volts)

TRACINGS

CONCLUSION

Sign. of the Student

Sign. of the faculty

EXPERIMENT: - 6

AIM OF THE EXPERIMENT

To study Three Phase Semi-controlled & Fully Controlled Rectifier circuit with R load.

APPARATUS REQUIRED


SL No.	Name of Apparatus	Specification	Quantity
01	3-phase Power modulator Kit		
02	DSO		
03	Ammeter, Voltmeter		
04	3-phase Variac		
05	Multi-meter		
06	Patch Chord/ Connecting leads		

THEORY

For any current to flow in the load at least one device from the top group (T_1, T_3, T_5) and one from the bottom group (T_2, T_4, T_6) must conduct. Then from symmetry consideration it can be argued that each thyristor conducts for 120° of the input cycle. Now the thyristors are fired in the sequence $T_1 \rightarrow T_2 \rightarrow T_3 \rightarrow T_4 \rightarrow T_5 \rightarrow T_6 \rightarrow T_1$ with 60° interval between each firing. Therefore, thyristors on the same phase leg are fired at an interval of 180° and hence cannot conduct simultaneously. This leaves only six possible conduction mode for the converter in the continuous conduction mode of operation. These are $T_1T_2, T_2T_3, T_3T_4, T_4T_5, T_5T_6, T_6T_1$. The output voltage is given by

$$V_0 = \frac{3\sqrt{2}}{\pi} V_L \cos\alpha$$

MODEL GRAPH

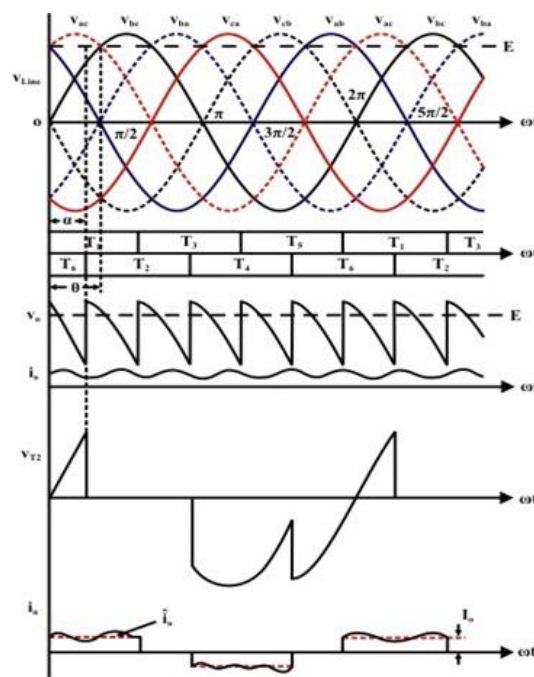

CIRCUIT DIAGRAM

PROCEDURE

1. The Connections were made as per the circuit diagram.
2. The voltmeter and DSO was connected across the load.
3. The potentiometer was kept at the minimum position.
4. AC source was switched on.
5. The output wave form was observed and the output voltage was calculated.

OBSERVATION TABLE

Sl. No.	Firing angle (α)	I/P Voltage (Volts)	O/P Voltage (Volts)

TRACINGS

CONCLUSION

Sign. of the Student

Sign. of the faculty

EXPERIMENT: - 7

AIM OF THE EXPERIMENT

To study of single Phase PWM Voltage Source Inverter.


APPARATUS REQUIRED

SLNo.	Name of Apparatus	Specification	Quantity
01	Power modulator Kit		
02	DSO		
03	Ammeter/Voltmeter		
04	Load		
05	Connecting Leads		

THEORY

The system consists of two independent circuits illustrating single-phase PWM voltage-sourced inverters. The Half-Bridge Converter block and the Full-Bridge converter block are modeling simplified model of an IGBT/Diode pair where the forward voltages of the forced-commutated device and diode are ignored. The converters are controlled in open loop with the PWM Generator blocks. The two circuits use the same DC voltage, carrier frequency and modulation index. Switches shown in the circuit diagrams are power electronics switches. For low voltage and low power applications power BJTs are used, for medium power applications power MOSFETs & power IGBTs are used and for high voltage and high-power applications power IGCTs are used.

MODEL GRAPH

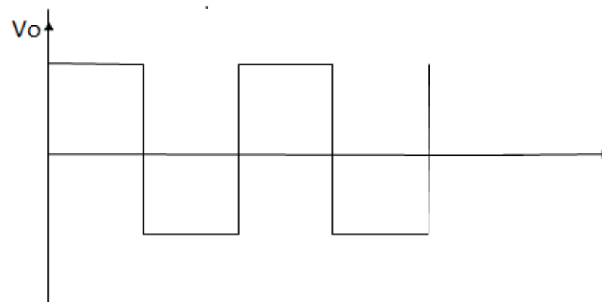

CIRCUIT DIAGRAM

PROCEDURE

1. The Connections were made as per the circuit diagram.
2. The voltmeter and DSO was connected across the load.
3. The output wave form was observed and the output voltage was calculated.
4. The carrier frequency was varied to obtain different values of output voltage and current.

OBSERVATION TABLE

Sl. No.	Frequency	O/P Current(A)	O/P Voltage (Volts)

TRACINGS**CONCLUSION****Sign. of the Student****Sign. of the faculty**

EXPERIMENT: - 8

AIM OF THE EXPERIMENT

To study of the fly back converter and forward converter.

APPARATUS REQUIRED

SL No.	Name of Apparatus	Specification	Quantity
1	MOSFET based Forward & Flyback Converter kit		
2	DC Regulated Power supply- 0-30V/2A (single)		
3	Rheostat- I00 ohms/2Amps.		
4	CRO		
5	Patch cords		

THEORY

Fly Back Converter:

A flyback converter is a very practical isolated version of the buck-boost converter. The inductor of the buck-boost converter has been replaced by a flyback transformer. The input dc source V_s and switch S are connected in series with the transformer primary. The diode D and the RC output circuit are connected in series with the secondary of the flyback transformer. When the switch S is on, the current in the magnetizing inductance increases linearly, the diode D is off and there is no current in the ideal transformer windings. When the switch is turned off, the magnetizing inductance current is diverted into the ideal transformer, the diode turns on, and the transformed magnetizing inductance current is supplied to the R-C load. The output voltage is given by

$$V_0 = V_s \times \frac{N_2}{N_1} \times \frac{D}{1-D}$$

Forward Converter:

When the switch S is on, diode D_1 conducts and diode D_2 is off. The energy is transferred from the input, through the transformer, to the output filter. When the switch S is off, the state of diodes D_1 and D_2 is reversed. In the forward converter, the energy-transfer current flows through the transformer in one direction. Hence, an additional winding with diode D_3 is needed to bring the magnetizing current of the transformer to zero, which prevents transformer saturation. The turns ratio $N_1=N_3$ should be selected in such a way that the magnetizing current decreases to zero during a fraction of the time interval when the switch S is off. The output voltage is given by

$$V_0 = V_s \times \frac{N_2}{N_1} \times D$$

CIRCUIT DIAGRAM

PROCEDURE

1. The Connections were made as per the circuit diagram.
2. The voltmeter and DSO was connected across the load.
3. The output voltage was recorded.

OBSERVATION TABLE

For flyback Converter:

SL. NO.	I/P Voltage (V_s)	Duty Cycle (%)	Load Voltage (V_o)

For forward Converter:

SL. NO.	I/P Voltage (V_s)	Duty Cycle (%)	Load Voltage (V_o)

TRACINGS

CONCLUSION

Sign. of the Student

Sign. of the faculty